

COL215 LAB Assignment 2 : Seven-Segment Display Logic

Mohit Sharma(2019CS10372), Arka Mandal(2019CS50617)

1 Aim

Design a combination circuit that takes a decimal/hexadecimal digit encoded using 4 bits and produces 7-bit output for seven segment displays of BASYS3 FPGA board. Do extensive simulation of the design using Xilinx simulator, and then implement the circuit on BASYS-3 FPGA board.

2 Combinational Logic Design

We have for input bit representing a hexadecimal number between 0 to f, and we need to map them to corresponding display symbol through 7 output bits of seven-segment display.

A(sw[3])	B(sw[2])	C(sw[1])	D(sw[0])	a	b	c	d	e	f	g	Display
0	0	0	0	1	1	1	1	1	1	0	0
0	0	0	1	0	1	1	0	0	0	0	1
0	0	1	0	1	1	0	1	1	0	1	2
0	0	1	1	1	1	1	1	0	0	1	3
0	1	0	0	0	1	1	0	0	1	1	4
0	1	0	1	1	0	1	1	0	1	1	5
0	1	1	0	1	0	1	1	1	1	1	6
0	1	1	1	1	1	1	0	0	0	0	7
1	0	0	0	1	1	1	1	1	1	1	8
1	0	0	1	1	1	1	1	0	1	1	9
1	0	1	0	1	1	1	0	1	1	1	A
1	0	1	1	0	0	1	1	1	1	1	b
1	1	0	0	1	0	0	1	1	1	0	C
1	1	0	1	0	1	1	1	1	0	1	d
1	1	1	0	1	0	0	1	1	1	1	E
1	1	1	1	1	0	0	0	1	1	1	F

From above mapping we created k-map for each segment to get the combinational logic equations.

As for basys board we need to set output bit 0 to glow the corresponding segment and 1 to not glow it, hence we have set :

seg[0] = not a;

seg[1] = not b;

seg[2] = not c;

seg[3] = not d;

seg[4] = not e;

seg[5] = not f;

seg[6] = not g;

Also anode bit corresponding to rightmost display is set to 0 and other to 1 so that only rightmost display glows.

(a)

AB \ CD	$\bar{C}\bar{D}$	$\bar{C}D$	$C\bar{D}$	CD
$\bar{A}\bar{B}$	1		1	1
$\bar{A}B$		1	1	1
AB	1		1	1
$A\bar{B}$	1	1		1

$$a = \bar{A}\bar{B}\bar{C} + \bar{A}B\bar{D} + A\bar{D} + \bar{A}C + BC + \bar{B}\bar{D}$$

(b)

	$\bar{C}\bar{D}$	$\bar{C}D$	$C\bar{D}$	CD
$\bar{A}\bar{B}$	1	1	1	1
$\bar{A}B$	1		1	
AB		1		
$A\bar{B}$	1	1		1

$$b = \bar{A}\bar{C}\bar{D} + \bar{A}C\bar{D} + A\bar{C}D + \bar{B}\bar{C} + \bar{B}\bar{D}$$

(c)

	$\bar{C}\bar{D}$	$\bar{C}D$	$C\bar{D}$	CD
$\bar{A}\bar{B}$	1	1	1	
$\bar{A}B$	1	1	1	1
AB		1		
$A\bar{B}$	1	1	1	1

$$c = \bar{A}\bar{C} + \bar{A}\bar{D} + \bar{C}D + \bar{A}B + AB$$

(d)

	$\bar{C}\bar{D}$	$\bar{C}D$	$C\bar{D}$	CD
$\bar{A}\bar{B}$	1		1	1
$\bar{A}B$		1		1
AB	1	1		1
$A\bar{B}$	1	1	1	

$$d = \bar{A}\bar{B}\bar{D} + \bar{B}CD + B\bar{C}D + BC\bar{D} + AC$$

(e)

	$\bar{C}\bar{D}$	$\bar{C}D$	CD	$C\bar{D}$
$\bar{A}\bar{B}$	1			1
$\bar{A}B$				1
AB	1	1	1	1
$A\bar{B}$	1		1	1

$$e = \bar{B}\bar{D} + \bar{C}\bar{D} + AC + AB$$

(f)

	$\bar{C}\bar{D}$	$\bar{C}D$	CD	$C\bar{D}$
$\bar{A}\bar{B}$	1			
$\bar{A}B$	1	1		1
AB	1		1	1
$A\bar{B}$	1	1	1	1

$$f = \bar{A}B\bar{C} + \bar{C}\bar{D} + B\bar{D} + A\bar{B} + AC$$

(g)


	$\bar{C}\bar{D}$	$\bar{C}D$	CD	$C\bar{D}$
$\bar{A}\bar{B}$			1	1
$\bar{A}B$	1	1		1
AB		1	1	1
$A\bar{B}$	1	1	1	1

$$g = \bar{A}BC + \bar{B}C + \bar{C}\bar{D} + A\bar{B} + AD$$

3 Simulation

 The code is simulated on test-bench created by the name test.vhd.





4 Utilisation Report

Utilisation report is also given in the submission.

4 LUT's are used

15 Input Output Blocks are used (4 switch inputs(sw) and 7 segment outputs(seg) and 4 display outputs(an))

5 Extra

We earlier tried to write the vhdl code using switch case as:

```
process(sw) is
begin
    case sw is
        when "0000" => seg <="1000000"; --0
        when "0001" => seg <="1111001"; --1
        when "0010" => seg <="0100100"; --2
        when "0011" => seg <="0110000"; --3
        when "0100" => seg <="0011001"; --4
        when "0101" => seg <="0010010"; --5
        when "0110" => seg <="0000010"; --6
        when "0111" => seg <="1111000"; --7
        when "1000" => seg <="0000000"; --8
        when "1001" => seg <="0010000"; --9
        when "1010" => seg <="0001000"; --a
        when "1011" => seg <="0000011"; --b
        when "1100" => seg <="1000110"; --c
        when "1101" => seg <="0100001"; --d
        when "1110" => seg <="0000110"; --e
        when "1111" => seg <="0001110"; --f
        when others => seg <="0111111";
    end case;
    an<="1110";
end process;
```

Though this is run sequentially but the resource utilisation is same as combinational circuit.